

实验项目名称: Function Units Design

一、实验目的和要求


Please do the project step by step according to the project tutorial. Design the basic function components including ALU, ALU Controller and register file using Xilinx.

二、实验内容和原理

Design the basic function components including ALU, ALU Controller and register file.

1. ALU

 - 1) Input: Operator r and s are 32-bit integers, and aluc is the code which defines ALU Operating.
- 2) Processing: $aluo = r \text{ op } s$; $zf = (op == sub) \& \& (r == s)$;
- 3) Output: aluo is the result of $(r \text{ op } s)$, zf is the flag of zero output.



2. ALU Controller


- 1) Input: 2-bit ALU Operation Code, 6-bit Function Code
- 2) Processing: mapping according to ALU Operation Code Table
- 3) Output: 3-bit ALU Controller



3. Register file

- 1) Input: Reading Address 1, Reading Address 2, Writing Address, Writing Data, Write Enable.

 - 2) Processing: According read or write instruction, output the operators.
- 3) Output: Operator 1, Operator 2.



三、 实验过程和数据记录

1. ALU

The code of the file “macro.vh” :

```
//macro.vh
//macro definitions
//ALU CONTROL CODES
`define ALU_CTL_AND 3'b000
`define ALU_CTL_OR 3'b001
`define ALU_CTL_ADD 3'b010
`define ALU_CTL_SUB 3'b110
`define ALU_CTL_SLT 3'b111
```

The code of the file “ALU.v” :

```
`include "macro.vh"
module ALU(input CCLK, input [2:0] SW, output LCDRS, LCDRW, LCDE, output
[3:0] LCDDAT, output LED);
    wire [3:0] lcdd;
    wire rslcd, rwlcd, elcd;
    wire o_zf; //o_zf: zero flag output
    wire [31:0] o_alu; //o_alu: ALU result
    wire [2:0] i_aluc; //i_aluc: ALU ctrl
    reg [31:0] o_alu_old; //o_alu_old: former ALU result
    reg [255:0] strdata; //strdata: data displayed in the LCD
    reg [31:0] i_r; //i_r: r input of ALU
    reg [31:0] i_s; //i_s: s input of ALU
    reg rst; //rst: reset signal indicating whether ALU result is updated

    assign LCDDAT[3]=lcdd[3];
    assign LCDDAT[2]=lcdd[2];
    assign LCDDAT[1]=lcdd[1];
    assign LCDDAT[0]=lcdd[0];
    assign LCDRS=rslcd;
    assign LCDRW=rwlc;
    assign LCDE=elcd;
    //output zero flag to LED
    assign LED = o_zf;
    //use switches as ALU ctrl input
```

```

assign i_aluc[0] = SW[0];
assign i_aluc[1] = SW[1];
assign i_aluc[2] = SW[2];

initial begin
    strdata = "1111 2222"; //set display data
    i_r = 32'h1111; //set r input
    i_s = 32'h2222; //set s input
    rst = 0; //set rst singal
    o_alu_old = 0; //set initial ALU's old result
end

display M0 (CCLK, rst, strdata, rslcd, rwlcd, elcd, lcdd);
single_alu M1(i_r, i_s, i_aluc, o_zf, o_alu);

always @(posedge CCLK) begin
    if (o_alu_old != o_alu) begin
        //display alu result in the LCD using sexadecimal notion
        if (o_alu[15:12] < 10)
            strdata[127:120] = 8'h30 + o_alu[15:12];
        else
            strdata[127:120] = 8'h61 + o_alu[15:12]-10;
        if (o_alu[11:8] < 10)
            strdata[119:112] = 8'h30 + o_alu[11:8];
        else
            strdata[119:112] = 8'h61 + o_alu[11:8]-10;
        if (o_alu[7:4] < 10)
            strdata[111:104] = 8'h30 + o_alu[7:4];
        else
            strdata[111:104] = 8'h61 + o_alu[7:4]-10;
        if (o_alu[3:0] < 10)
            strdata[103:96] = 8'h30 + o_alu[3:0];
        else
            strdata[103:96] = 8'h61 + o_alu[3:0]-10;
        rst = 1;
        o_alu_old = o_alu; //update alu result
    end
    else
        rst = 0;
    end
endmodule

```

The code of the file “single_alu.v” :

```

`include "macro.vh"
module single_alu(i_r,i_s,i_aluc,o_zf,o_alu);
    input [31:0] i_r; //i_r: r input
    input [31:0] i_s; //i_s: s input
    input [2:0] i_aluc; //i_aluc: ctrl input
    output o_zf; //o_zf: zero flag output
    output [31:0] o_alu; //o_alu: alu result output
    reg o_zf;
    reg [31:0] o_alu;

    always @(i_aluc or i_r or i_s) begin
        case (i_aluc)
            `ALU_CTL_AND:begin
                o_zf=0;
                o_alu=i_r & i_s;
            end
            `ALU_CTL_OR:begin
                o_zf=0;

```

```

        o_alu=i_r | i_s;
    end
    `ALU_CTL_ADD:begin
        o_zf=0;
        o_alu=i_r + i_s;
    end
    `ALU_CTL_SUB:begin
        o_alu=i_r - i_s;
        o_zf=(o_alu == 0);
    end
    `ALU_CTL_SLT:begin
        o_zf=0;
        if(i_r < i_s)
            o_alu=1;
        else o_alu=0;
        end
    default:begin
        o_zf=0;
        o_alu=0;
    end
endcase
end
endmodule

```

2. ALU Controller

The code of the file “ALUC.v” :

```

`include "macro.vh"
module ALUC(input CCLK, input [1:0]BTN, input [3:0] SW, output LCDRS, LCDRW,
LCDE, output [3:0] LCDDAT, output LED);
    wire [3:0] lcdd;
    wire rslcd, rwlcd, elcd;
    wire o_zf; //o_zf: zero flag output
    wire [31:0] o_alu; //o_alu: ALU result
    wire [2:0] i_aluc; //i_aluc: ALU ctrl signal
    wire [1:0] alu_op; //alu_op: the op field of ALU ctrl input signal
    wire [3:0] func; //func: the function field of ALU ctrl input signal
    reg [31:0] o_alu_old; //o_alu_old: former ALU result
    reg [255:0] strdata; //strdata: data displayed in the LCD
    reg [31:0] i_r; //i_r: r input of ALU
    reg [31:0] i_s; //i_s: s input of ALU
    reg rst; //rst: reset signal indicating whether ALU result is updated

    assign LCDDAT[3] = lcdd[3];
    assign LCDDAT[2] = lcdd[2];
    assign LCDDAT[1] = lcdd[1];
    assign LCDDAT[0] = lcdd[0];
    assign LCDRS = rslcd;
    assign LCDRW = rwlcd;
    assign LCDE = elcd;
    //output zero flag to LED
    assign LED = o_zf;
    //use switches as func input
    assign func[0] = SW[0];
    assign func[1] = SW[1];
    assign func[2] = SW[2];

```

```

assign func[3] = SW[3];
//use buttons as alu_op input
assign alu_op[0] = BTN[0];
assign alu_op[1] = BTN[1];

initial begin
    strdata = "1111 2222"; //set display data
    i_r = 32'h1111; //set r input
    i_s = 32'h2222; //set s input
    rst = 0; //set rst singal
    o_alu_old = 0; //set initial ALU's old result
end

display M0 (CCLK, rst, strdata, rslcd, rwlcd, elcd, lcdd);
single_alu M1(i_r, i_s, i_aluc, o_zf, o_alu);
single_aluc M2(alu_op, func, i_aluc);

always @(posedge CCLK) begin
    //display alu result in the LCD using sexadecimal notion
    if (o_alu_old != o_alu) begin
        if (o_alu[15:12] < 10)
            strdata[127:120] = 8'h30 + o_alu[15:12];
        else
            strdata[127:120] = 8'h61 + o_alu[15:12]-10;
        if (o_alu[11:8] < 10)
            strdata[119:112] = 8'h30 + o_alu[11:8];
        else
            strdata[119:112] = 8'h61 + o_alu[11:8]-10;
        if (o_alu[7:4] < 10)
            strdata[111:104] = 8'h30 + o_alu[7:4];
        else
            strdata[111:104] = 8'h61 + o_alu[7:4]-10;
        if (o_alu[3:0] < 10)
            strdata[103:96] = 8'h30 + o_alu[3:0];
        else
            strdata[103:96] = 8'h61 + o_alu[3:0]-10;
        rst = 1;
        o_alu_old = o_alu; //update alu result
    end
    else
        rst = 0;
end

endmodule

```

The code of the file “ALU.v” :

```

//macro definitions of instruction types
`define ALUC_CTL_AND 3'b000
`define ALUC_CTL_OR 3'b001
`define ALUC_CTL_ADD 3'b010
`define ALUC_CTL_SUB 3'b110
`define ALUC_CTL_SLT 3'b111
`define RTYPE_ADD 4'b0000
`define RTYPE_SUB 4'b0010
`define RTYPE_SLT 4'b1010
`define RTYPE_AND 4'b0100

```

```

`define RTYPE_OR      4'b0101
`define RTYPE_XOR     4'b0110
`define RTYPE_NOR     4'b0111
`define RTYPE_ADDU    4'b0001
`define RTYPE_SLTU    4'b1011
`include "macro.vh"
module single_aluc(aluop, func, aluc);
    input [1:0] aluop; //alu_op: the op field of ALU ctrl input signal
    input [5:0] func; //func: the function field of ALU ctrl input signal
    output [2:0] aluc; //i_aluc: ALU ctrl signal
    reg [2:0] aluc;

    always @(aluop or func) begin
        case (aluop)
            2'b00:begin
                aluc=`ALU_CTL_ADD;
            end
            2'b01:begin
                aluc=`ALU_CTL_SUB;
            end
            2'b1x:begin
                case(func)
                    `RTYPE_AND:aluc=`ALU_CTL_AND;
                    `RTYPE_OR:aluc=`ALU_CTL_OR;
                    `RTYPE_ADD:aluc=`ALU_CTL_ADD;
                    `RTYPE_SUB:aluc=`ALU_CTL_SUB;
                    `RTYPE_SLT:aluc=`ALU_CTL_SLT;
                    default:aluc=3'b000;
                endcase
            end
            default:aluc=3'b000;
        endcase
    end
endmodule

```

The “macro.vh” and “single_alu.v” file is the same as those in the ALU project.

3. Register file

```

//macro definitions of instruction types
`define ALUC_CTL_AND 3'b000
`define ALUC_CTL_OR 3'b001
`define ALUC_CTL_ADD 3'b010
`define ALUC_CTL_SUB 3'b110
`define ALUC_CTL_SLT 3'b111
`define RTYPE_ADD 4'b0000
`define RTYPE_SUB 4'b0010
`define RTYPE_SLT 4'b1010
`define RTYPE_AND 4'b0100
`define RTYPE_OR 4'b0101
`define RTYPE_XOR 4'b0110
`define RTYPE_NOR 4'b0111

```

```

`define RTYPE_ADDU    4'b0001
`define RTYPE_SLTU    4'b1011

module Rtype(clk, rst, instru, Adat, Bdat, result);
    input clk;                //clk: clock signal
    input rst;                //rst: reset signal
    input [31:0] instru;      //instru: instruction input
    //result: ALU result output
    //Adat: data of ALU's A input
    //Bdat: data of ALU's B input
    output [31:0] result, Adat, Bdat;
    wire [31:0] result;
    wire [31:0] Wdat, Adat, Bdat, ALUout;
    wire [2:0] ALUoper;

    RegFile x_regfile(clk, instru[25:21], instru[20:16], instru[15:11],
result, Adat, Bdat, 1);
    ALUctr x_aluctr(2'b10, instru[5:0], ALUoper);
    ALUnit x_alunit(Adat, Bdat, ALUoper, result, zero);
endmodule

module ALUnit(Adat, Bdat, ALUoper, Result, zero);
    input [31:0] Adat;        //Adat: data of A input
    input [31:0] Bdat;        //Bdat: data of B input
    input [2:0] ALUoper;      //ALUoper: ALU ctrl signal
    output [31:0] Result;     //Result: ALU result output
    reg [31:0] Result;
    output zero;
    reg zero;

    always @(ALUoper)begin
        case(ALUoper)
            3'b000: Result=Adat & Bdat;           //And
            3'b001: Result=Adat | Bdat;           //Or
            3'b010: Result=Adat + Bdat;           //Add
            3'b110: Result=Adat - Bdat;           //Sub
            3'b111: if(Adat < Bdat) Result=1;     //Slt
                     else Result=0;
        endcase
        if(Adat == Bdat)zero=1; else zero=0;
    end
endmodule

module ALUctr(ALUop, Func, ALUoper);
    input [1:0] ALUop;        //ALUop: the op field of ALU ctrl input signal
    input [5:0] Func;         //Func: the function field of ALU ctrl input signal
    output [2:0] ALUoper;     //ALUoper: ALU ctrl signal
    reg [2:0] ALUoper;

    always @ (ALUop or Func)begin
        case(ALUop)
            2'b00: ALUoper = 3'b010;             //Add
            2'b01: ALUoper = 3'b110;             //Sub
            default:
                case(Func)
                    6'b100000: ALUoper = 3'b010; //Add
                    6'b100010: ALUoper = 3'b110; //Sub
                    6'b100100: ALUoper = 3'b000; //And
                    6'b100101: ALUoper = 3'b001; //Or
                    6'b101010: ALUoper = 3'b111; //Slt
                endcase
        endcase
    end
endmodule

```

```

        endcase
    end
endmodule

module RegFile(clk, regA, regB, regW, Wdat, Adat, Bdat, RegWrite);
    input clk;           //clk: clock signal
    input [4:0] regA;     //regA: index of register A
    input [4:0] regB;     //regB: index of register B
    input [4:0] regW;     //regW: index of register to write into
    input [31:0] Wdat;    //Wdat: the data to write into regW
    input RegWrite;       //RegWrite: enable signal of writing
    //Adat: the content of regA
    //Bdat: the content of regB
    output [31:0] Adat, Bdat;
    reg [31:0] Adat, Bdat;
    //register file
    reg[31:0] Szero, Sat, Sa0, Sa1, Sv0, Sv1, Sv2, Sv3; //0
    reg[31:0] St0, St1, St2, St3, St4, St5, St6, St7; //8
    reg[31:0] Ss0, Ss1, Ss2, Ss3, Ss4, Ss5, Ss6, Ss7; //16
    reg[31:0] St8, St9, Sk0, Sk1, Sgp, Sfp, Ssp, Sra; //24

    initial begin
        Szero = 0; //register file
        Sat = 1;
        Sa0 = 2;
        Sa1 = 3;
        Sv0 = 4;
        Sv1 = 5;
        Sv2 = 6;
        Sv3 = 7;
        St0 = 8;
        St1 = 9;
        St2 = 10;
        St3 = 11;
        St4 = 12;
        St5 = 13;
        St6 = 14;
        St7 = 15;
        Ss0 = 16;
        Ss1 = 17;
        Ss2 = 18;
        Ss3 = 19;
        Ss4 = 20;
        Ss5 = 21;
        Ss6 = 22;
        Ss7 = 23;
        St8 = 24;
        St9 = 25;
        Sk0 = 26;
        Sk1 = 27;
        Sgp = 28;
        Sfp = 29;
        Ssp = 30;
        Sra = 31;
    end

    always @ (posedge clk)begin
        case(regA)
            //read the content of regA
            0:      Adat = 0;
            1:      Adat = Sat ;
            2:      Adat = Sa0 ;

```



```

3:      Adat = Sa1 ;
4:      Adat = Sv0 ;
5:      Adat = Sv1 ;
6:      Adat = Sv2 ;
7:      Adat = Sv3 ;
8:      Adat = St0 ;
9:      Adat = St1 ;
10:     Adat = St2 ;
11:     Adat = St3 ;
12:     Adat = St4 ;
13:     Adat = St5 ;
14:     Adat = St6 ;
15:     Adat = St7 ;
16:     Adat = Ss0 ;
17:     Adat = Ss1 ;
18:     Adat = Ss2 ;
19:     Adat = Ss3 ;
20:     Adat = Ss4 ;
21:     Adat = Ss5 ;
22:     Adat = Ss6 ;
23:     Adat = Ss7 ;
24:     Adat = St8 ;
25:     Adat = St9 ;
26:     Adat = Sk0 ;
27:     Adat = Sk1 ;
28:     Adat = Sgp ;
29:     Adat = Sfp ;
30:     Adat = Ssp ;
31:     Adat = Sra ;
endcase
case(regB)
//read the content of regB
0:      Bdat = 0;
1:      Bdat = Sat ;
2:      Bdat = Sa0 ;
3:      Bdat = Sa1 ;
4:      Bdat = Sv0 ;
5:      Bdat = Sv1 ;
6:      Bdat = Sv2 ;
7:      Bdat = Sv3 ;
8:      Bdat = St0 ;
9:      Bdat = St1 ;
10:     Bdat = St2 ;
11:     Bdat = St3 ;
12:     Bdat = St4 ;
13:     Bdat = St5 ;
14:     Bdat = St6 ;
15:     Bdat = St7 ;
16:     Bdat = Ss0 ;
17:     Bdat = Ss1 ;
18:     Bdat = Ss2 ;
19:     Bdat = Ss3 ;
20:     Bdat = Ss4 ;
21:     Bdat = Ss5 ;
22:     Bdat = Ss6 ;
23:     Bdat = Ss7 ;
24:     Bdat = St8 ;
25:     Bdat = St9 ;
26:     Bdat = Sk0 ;
27:     Bdat = Sk1 ;
28:     Bdat = Sgp ;

```

```

        29:    Bdat = Sfp ;
        30:    Bdat = Ssp ;
        31:    Bdat = Sra ;
    endcase
end
always @ (negedge clk)begin
    if(RegWrite==1)
        case(Wdat)
            //write Wdat into the register file
            0:    Szero = 0;
            1:    Sat = Wdat;
            2:    Sa0 = Wdat;
            3:    Sa1 = Wdat;
            4:    Sv0 = Wdat;
            5:    Sv1 = Wdat;
            6:    Sv2 = Wdat;
            7:    Sv3 = Wdat;
            8:    St0 = Wdat;
            9:    St1 = Wdat;
            10:   St2 = Wdat;
            11:   St3 = Wdat;
            12:   St4 = Wdat;
            13:   St5 = Wdat;
            14:   St6 = Wdat;
            15:   St7 = Wdat;
            16:   Ss0 = Wdat;
            17:   Ss1 = Wdat;
            18:   Ss2 = Wdat;
            19:   Ss3 = Wdat;
            20:   Ss4 = Wdat;
            21:   Ss5 = Wdat;
            22:   Ss6 = Wdat;
            23:   Ss7 = Wdat;
            24:   St8 = Wdat;
            25:   St9 = Wdat;
            26:   Sk0 = Wdat;
            27:   Sk1 = Wdat;
            28:   Sgp = Wdat;
            29:   Sfp = Wdat;
            30:   Ssp = Wdat;
            31:   Sra = Wdat;
        endcase
    end
endmodule

```

四、 实验结果分析

1. ALU:

The following table is the lab result (r input of ALU is 1111, s input of ALU is 2222) :

the status of switches	ALU operation	ALU result displayed in the LCD
000	AND	0000
001	OR	3333

010	ADD	3333
110	SUB	eeef
111	SLT	0001

The result indicates that the code functions correx

2. ALU Controller:

The following table is the lab result (r input of ALU is 1111, s input of ALU is 2222) :

the status of buttons	the status of switches	ALU operation	ALU result
00	xxxx	ADD	3333
01	xxxx	SUB	eeef
1x	0000	ADD	3333
1x	0010	SUB	eeef
1x	0100	AND	0000
1x	0101	OR	3333
1x	1010	SLT	0001

The result indicates that the code functions correctly.

3. Register file:

The code of the test fixture file:

```

module test;
    // Inputs
    reg clk;
    reg rst;
    reg [31:0] instru;
    // Outputs
    wire [31:0] Adat;
    wire [31:0] Bdat;
    wire [31:0] result;
    parameter ON_delay=80, OFF_delay=80;
    // Instantiate the Unit Under Test (UUT)
    Rtype uut (
        .clk(clk),
        .rst(rst),
        .instru(instru),
        .Adat(Adat),
        .Bdat(Bdat),
        .result(result)
    );

    always begin
        clk =1;
    end

```


```

        #ON_delay;
        clk =0;
        #OFF_delay;
    end

    initial begin
        rst=1;
        instru=32'h01A88020;           //ADD    $S0 , $T5 , $T0
        #160  instru=32'h01C98822;     //SUB    $S1 , $T6 , $T1
        #160  instru=32'h01EA9024;     //AND    $S2 , $T7 , $T2
        #160  instru=32'h030B9825;     //OR     $S3 , $T8 , $T3
        #160  instru=32'h032CA02A;     //SLT   $S4 , $T9 , $T4
        #500  $dumpflush;
        $stop;
    end
end
endmodule

```

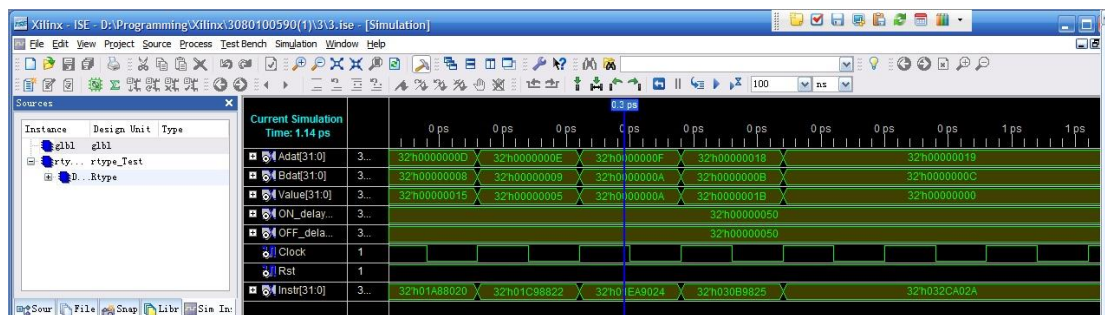The following picture is the result of simulation:




The result indicates that the code functions correctly.

五、 讨论与心得

The task of this lab is not hard and I've finished coding early, but I've met some other troubles.

At first I couldn't pass the "Map" step. Then I checked my error and found that I've set a wrong device which led to the definition in the UCF file is not correspondent with the actual hardware port. So I corrected the device to XC3S500E and got the correct result.

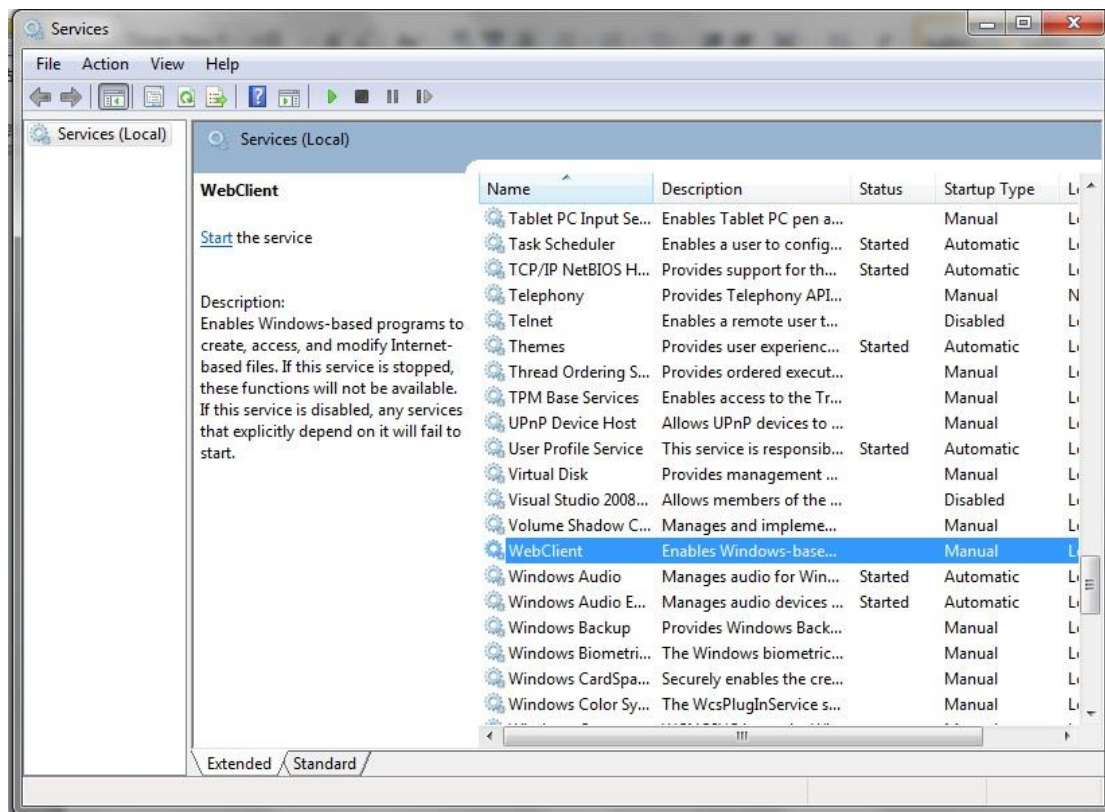Another trouble is the error I met when running simulation. I've checked my codes many times and made sure there was nothing wrong in it, so I searched the error in the Internet. The solution is to open the WebClient services:



Because I have no root authority to open it, so I have to finished my simulation in another PC.